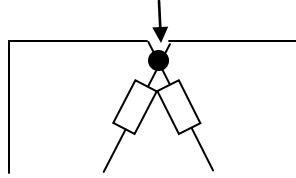


Use 2 matched resistors to make this bridge, 2k ohm works good.

Twist and solder together



Insulate the legs so they don't touch together.

AIN 5	+ DR	DR-	AIN 6
386A	384A	385A	387A

